
Contents

Preface	ix
Chapter 1. Latch and Flip-Flop	1
1.1. Introduction	1
1.2. General overview	1
1.2.1. SR latch	6
1.2.2. $\bar{S} \bar{R}$ latch	9
1.2.3. Application: switch debouncing	11
1.3. Gated SR latch	11
1.3.1. Implementation based on an SR latch	12
1.3.2. Implementation based on an $\bar{S} \bar{R}$ latch	14
1.4. Gated D latch	15
1.5. Basic JK flip-flop	16
1.6. T flip-flop	18
1.7. Master-slave and edge-triggered flip-flop	20
1.7.1. Master-slave flip-flop	20
1.7.2. Edge-triggered flip-flop	24
1.8. Flip-flops with asynchronous inputs	30
1.9. Operational characteristics of flip-flops	33
1.10. Exercises	34
1.11. Solutions	39
Chapter 2. Binary Counters	51
2.1. Introduction	51
2.2. Modulo 4 counter	52
2.3. Modulo 8 counter	53
2.4. Modulo 16 counter	55
2.4.1. Modulo 10 counter	57

2.5. Counter with parallel load	60
2.6. Down counter	62
2.7. Synchronous reversible counter	64
2.8. Decoding a down counter	65
2.9. Exercises	66
2.10. Solutions	73
Chapter 3. Shift Register	85
3.1. Introduction	85
3.2. Serial-in shift register	85
3.3. Parallel-in shift register	85
3.4. Bidirectional shift register	88
3.5. Register file	90
3.6. Shift register based counter	91
3.6.1. Ring counter	92
3.6.2. Johnson counter	93
3.6.3. Linear feedback counter	94
3.7. Exercises	101
3.8. Solutions	107
Chapter 4. Arithmetic and Logic Circuits	117
4.1. Introduction	117
4.2. Adder	117
4.2.1. Half adder	117
4.2.2. Full adder	119
4.2.3. Ripple-carry adder	120
4.2.4. Carry-lookahead adder	122
4.2.5. Carry-select adder	124
4.2.6. Carry-skip adder	125
4.3. Comparator	127
4.4. Arithmetic and logic unit	129
4.5. Multiplier	136
4.5.1. Multiplier of 2-bit unsigned numbers	136
4.5.2. Multiplier of 4-bit unsigned numbers	137
4.5.3. Multiplier for signed numbers	138
4.6. Divider	143
4.7. Exercises	149
4.8. Solutions	158
Chapter 5. Digital Integrated Circuit Technology	177
5.1. Introduction	177
5.2. Characteristics of the technologies	177

5.2.1. Supply voltage	177
5.2.2. Logic levels	178
5.2.3. Immunity to noise	178
5.2.4. Propagation delay	179
5.2.5. Electric power consumption	179
5.2.6. Fan-out or load factor	179
5.3. TTL logic family	180
5.3.1. Bipolar junction transistor	180
5.3.2. TTL NAND gate	181
5.3.3. Integrated TTL circuit	182
5.4. CMOS logic family	183
5.4.1. MOSFET transistor	183
5.4.2. CMOS logic gates	184
5.5. Open drain logic gates	185
5.5.1. Three-state buffer	187
5.5.2. CMOS integrated circuit	188
5.6. Other logic families	189
5.7. Interfacing circuits of different technologies	189
5.8. Exercises	190
5.9. Solutions	193
Chapter 6. Semiconductor Memory	195
6.1. Introduction	195
6.2. Memory organization	195
6.3. Operation of a memory	197
6.4. Types of memory	199
6.4.1. Non-volatile memory	199
6.4.2. Volatile memories	202
6.4.3. Characteristics of the different memory types	207
6.5. Applications	207
6.5.1. Memory organization	208
6.5.2. Applications	209
6.6. Other types of memory	218
6.6.1. Ferromagnetic RAM	220
6.6.2. Content-addressable memory	222
6.6.3. Sequential access memory	223
6.7. Exercises	226
6.8. Solutions	230
Chapter 7. Programmable Logic Circuits	245
7.1. General overview	245
7.2. Programmable logic device	246
7.3. Applications	255

7.3.1. Implementation of logic functions	255
7.3.2. Two-bit adder	257
7.3.3. Binary-to-BCD and BCD-to-binary converters	263
7.4. Programmable logic circuits (CPLD and FPGA)	263
7.4.1. Principle and technology	264
7.4.2. CPLD	268
7.4.3. FPGA	270
7.5. References	274
7.6. Exercises	275
7.7. Solutions	284
Appendix	307
Bibliography	309
Index	311