
Contents

Introduction	ix
Chapter 1. Fundamentals of Sensing and Signal Conditioning	1
1.1. Introduction	1
1.2. Voltage generating sensors	1
1.2.1. General description	1
1.2.2. Examples	2
1.3. Current generating sensors	9
1.3.1. General description	9
1.3.2. Examples	10
1.3.3. Conditioning circuits	15
1.4. Charge generating sensors	19
1.4.1. General description	19
1.4.2. Examples	20
1.4.3. Conditioning	22
1.5. Resistive sensors	24
1.5.1. Examples	25
1.5.2. Caveats	29
1.5.3. Signal conditioning: measuring the total resistance	29
1.5.4. Measuring a resistance variation: the Wheatstone bridge	31
1.6. Reactive sensors	36
1.7. Conclusion	37

Chapter 2. Amplification and Amplifiers	39
2.1. Introduction	39
2.2. Introduction to operational amplifiers	40
2.2.1. The operational amplifier as a differential amplifier	40
2.2.2. Modeling ideal operational amplifiers	41
2.3. Limitations of real operational amplifiers	42
2.3.1. Saturation and rail-to-rail operational amplifiers	42
2.3.2. Input offset	43
2.3.3. Common mode rejection ratio	44
2.3.4. Bias currents	44
2.3.5. Stability and frequency response	45
2.3.6. Examples	46
2.4. Instrumentation amplifiers	47
2.4.1. Introduction	47
2.4.2. Differential amplifier with one operational amplifier	48
2.4.3. Differential amplifier with two operational amplifiers	51
2.4.4. Differential amplifier with three operational amplifiers	53
2.5. Isolation amplifiers	57
2.6. Conclusion	59
Chapter 3. Elements of Active Filter Synthesis	61
3.1. Introduction	61
3.2. Low-pass filter approximation	64
3.2.1. Aliasing in sampled systems and anti-aliasing filters	64
3.2.2. Definitions	65
3.2.3. All-pole filters: normalization and factorization	66
3.2.4. Butterworth approximation	69
3.2.5. Chebyshev approximation	71
3.2.6. Bessel–Thompson approximation	73
3.2.7. Examples	75
3.3. Active filter synthesis by means of standard cells	76
3.3.1. Low-pass Sallen-Key cell: a pair of complex conjugate poles	77
3.3.2. Low-pass active RC cell: a real negative pole	79

3.3.3. Cell order	80
3.4. Frequency transform techniques	82
3.4.1. High-pass filters	83
3.4.2. Band-pass filters	84
3.4.3. Band-reject (notch) filters	85
3.4.4. High-pass and band-pass cells	86
3.5. Conclusion	88
Chapter 4. Analog to Digital Converters	89
4.1. Digital to analog converters and analog to digital converters: an introduction	89
4.2. Notations and digital circuits	91
4.3. Sample and hold circuits	94
4.4. Converter structures	96
4.4.1. General features	96
4.4.2. Flash ADCs	98
4.4.3. A simple DAC: R2R ladder	101
4.4.4. Half-flash and pipeline ADCs	102
4.4.5. Successive approximation converters	104
4.4.6. Single- and double-ramp converters	106
4.4.7. Sigma-delta converters	110
4.5. No silver bullet: choosing the best trade-off	112
4.5.1. Conversion errors and artifacts	112
4.5.2. Performances of typical converters	114
4.6. Conclusion	118
Chapter 5. Introduction to Noise Analysis in Low Frequency Circuits	121
5.1. What is noise?	121
5.2. Stochastic modeling of a noise	123
5.2.1. Some definitions	123
5.2.2. Measurement units for $p_B(b)$ and $\Gamma_B(f)$	127
5.2.3. Negative and positive frequencies	128
5.3. Different kinds of stochastic noises	129
5.3.1. Thermal noise (Johnson–Nyquist)	130
5.3.2. Flicker or $1/f$ noise	131
5.3.3. Avalanche or breakdown noise	132

5.3.4. Burst or “popcorn” or random telegraph signal noise	132
5.3.5. Shot noise or Poisson noise	133
5.4. Limits of modeling	134
5.5. Contributions from stochastically independent noise sources	135
5.6. Noise equivalent bandwidth and noise factor	137
5.7. Amplifiers and noise	139
5.7.1. Noise models of operational amplifiers	139
5.7.2. Example: noise factor of a non-inverting amplifier	142
5.7.3. Noise models of instrumentation amplifiers	147
5.8. Noise from “outer space”: electromagnetic compatibility	148
5.9. Conclusion	152
Appendix	153
Bibliography	155
Index	157