
Contents

CHAPTER 1. GENERAL PROPERTIES OF MULTILEVEL CONVERTERS	1
1.1. Time-domain: multilevel waveform and apparent switching frequency.	1
1.2. Frequency domain: harmonic cancellation.	4
1.3. Transient response	5
1.4. Conclusion.	6
CHAPTER 2. TOPOLOGIES OF MULTILEVEL DC/DC CONVERTERS	9
2.1. Series connection	9
2.1.1. Direct series connection with isolated sources	9
2.1.2. Flying capacitor.	11
2.2. Parallel connection	14
2.2.1. Interleaved choppers with star-connected inductors	14
2.2.2. Interleaved choppers with InterCell Transformers (ICTs).	17
2.3. Series-parallel connection	20

CHAPTER 3. CONCEPT OF VECTORIZATION IN PLECS	23
3.1. Vectorized components	23
3.2. Star-connection block and parallel multicell converter	25
3.3. Series connection block and series multicell converter.	27
3.4. Generalized multicell commutation cell	28
3.5. Practice.	34
3.5.1. How to?	34
3.5.2. Basic blocks	34
CHAPTER 4. VECTORIZED MODULATOR FOR MULTILEVEL CHOPPERS.	37
4.1. General principle	37
4.2. xZOH: equalizing multisampler for multilevel choppers	38
4.2.1. Control as the main source of perturbation	38
4.2.2. Handling duty cycle variation	38
4.2.3. Frequency response of the equalizing sampler and modulator	51
4.3. Practice.	53
CHAPTER 5. VOLTAGE BALANCE IN SERIES MULTILEVEL CONVERTERS	57
5.1. Basic principles	57
5.2. Linear circuits	58
5.2.1. Internal balancers	58
5.2.2. External balance boosters	59
5.2.3. Pros and cons of internal/ external balance boosters	64
5.3. Nonlinear variants	65
5.3.1. Internal balance boosters	65
5.3.2. External balance boosters	66
5.4. Loss-based design.	67
5.4.1. Introduction	67
5.4.2. Internal balance boosters	68
5.4.3. External balance boosters	68
5.5. Vectorized models of balance boosters	69

CHAPTER 6. FILTER DESIGN.	75
6.1. Requirements	75
6.1.1. Steady state: current ripple, voltage ripple and standards	75
6.1.2. Transients	83
6.1.3. Extra design constraints	84
6.2. Design process	85
CHAPTER 7. DESIGN OF MAGNETIC COMPONENTS FOR MULTILEVEL CHOPPERS.	89
7.1. Requirements and problem formulation	89
7.2. Area product	92
7.2.1. Low frequency – low ripple formulation for filtering inductors.	92
7.2.2. General formulation for filtering inductors	94
7.2.3. Application to inductors for interleaved converters	95
7.2.4. Extension to InterCell Transformers.	97
7.3. Optimal area product of magnetic components for interleaved converters	99
7.3.1. Optimal area product for inductors.	99
7.3.2. Optimal area product for InterCell Transformers	101
7.4. Weight-optimal dimensions for a given area product	101
7.4.1. For inductors	101
7.4.2. For InterCell Transformers	107
7.5. Volume-optimal dimensions for a given area product.	118
7.6. Number of turns and air gap	120
7.7. Accounting for current overload	123
7.8. Optimal phase sequence for InterCell Transformers	123
7.9. Vectorized reluctance model of magnetics	125
7.9.1. Inductors	125
7.9.2. Cyclic cascade InterCell Transformers	126

7.9.3. Monolithic InterCell Transformers	128
7.10. Design process	130
CHAPTER 8. CLOSED-LOOP CONTROL OF MULTILEVEL DC/DC CONVERTERS.	131
8.1. Principle	131
8.2. Corresponding PLECS block.	133
8.3. Average model of the macro-commutation cell for transient studies	136
8.4. Conclusion.	140
BIBLIOGRAPHY	141
INDEX.	145