

---

## Contents

---

<b>Preface</b> . . . . .	ix
<b>Chapter 1. On Analog Circuits</b> . . . . .	1
1.1. Introduction: miscellaneous . . . . .	1
1.1.1. SPICE. . . . .	1
1.1.2. Technologies: conception-aided design . . . . .	5
1.1.3. Resistor technologies. . . . .	12
1.2. A simple but realistic amplifier circuit: the bipolar junction transistor with a common emitter. . . . .	19
1.2.1. Small signal equivalent schematic of common feedback emitter with base bridge. . . . .	20
1.2.2. Current gain calculation . . . . .	21
1.3. Integrated circuit design . . . . .	22
1.4. Current sources . . . . .	23
1.4.1. Simple current sources. . . . .	23
1.4.2. Wildar current source . . . . .	24
1.4.3. Wilson current source . . . . .	24
1.4.4. Current source and voltage source . . . . .	27
1.4.5. Advantages and disadvantages of both sources: one phase and Wildar. . . . .	28
1.4.6. Cascode-connected current source. . . . .	33
1.4.7. Single current source . . . . .	34
1.4.8. Improved Wilson current source . . . . .	35
1.5. A historic circuit: the 741 operational amplifier . . . . .	35
1.5.1. Active charge . . . . .	37

1.5.2. 741 description . . . . .	38
1.5.3. Continuous analysis . . . . .	39
1.5.4. Analysis of 741 small signals. . . . .	45
1.5.5. The third stage. . . . .	52
1.5.6. Considering the effect of the second order: computer analysis . . . . .	57
1.6. Electric simulator . . . . .	59
1.6.1. Analysis of steady-state linear circuits . . . . .	61
1.6.2. Transitional analysis . . . . .	66
1.6.3. Nonlinear system: Newton–Raphson method . . . . .	71
1.7. Simulation of a system with several active devices . . . . .	88
1.8. Basic analog functional blocks in (C)MOS technology . . . . .	107
1.8.1. Common source NMOS transistors . . . . .	107
1.8.2. Reminder on the general structure of the operational amplifier . . . . .	118
1.9. Conclusion . . . . .	146
 <b>Chapter 2. Noise and Interference in Mixed Circuits</b> . . . . .	147
2.1. Introduction . . . . .	147
2.2. Ground or power supply noise and substrate coupling . . . . .	148
2.2.1. Noise propagation in a silicon substrate. . . . .	150
2.2.2. Simulation methodology. . . . .	152
2.3. Noise in integrated oscillator circuits. . . . .	160
2.3.1. Oscillator design considerations . . . . .	160
2.3.2. VCO topography . . . . .	161
2.3.3. Results and discussion . . . . .	166
2.4. Sensitivity functions. . . . .	171
2.5. New developments in impulse sensitivity function . . . . .	177
2.5.1. Oscillators: brief recap of the theory . . . . .	177
2.5.2. Pulse sensitivity function (with some recap) . . . . .	181
2.5.3. Influence of digital blocks on analog blocks . . . . .	193
 <b>Chapter 3. From 2D to 3D: Opportunities and Challenges</b> . . . . .	207
3.1. Introduction . . . . .	207
3.2. 3D integration . . . . .	208
3.2.1. 3D impedance extraction . . . . .	215
3.2.2. Model validation . . . . .	224
3.2.3. Interconnections: compact models . . . . .	233

3.2.4. Validation: test structures . . . . .	235
3.2.5. Numerical simulations . . . . .	241
3.2.6. Prospects and future directions . . . . .	248
3.3. Conclusion . . . . .	249
<b>References . . . . .</b>	<b>251</b>
<b>Index . . . . .</b>	<b>253</b>