
Contents

Foreword	xi
Hugues GENEVOIS	
Photo Credits	xiii
Introduction	xv
Chapter 1. Ondes 1928	1
1.1. Presentation	1
1.2. Principle of operation	3
1.3. The diagram	4
1.4. Construction of a model of the “1928” ondes	8
1.4.1. The box	8
1.4.2. Construction.	9
1.4.3. The tuning capacitor controlled by a wire	10
1.4.4. The intensity key	14
1.5. Tests	18
1.5.1. Energy sources	18
1.5.2. The wiring	18
1.5.3. Tuning capacitor calibration	20
1.5.4. Adjusting the instrument	21
1.6. Perspectives of evolution	22
Chapter 2. Ondes No. 15 (1930)	23
2.1. Introduction	23
2.2. Presentation	23
2.3. Organization of the instrument	24
2.4. The heterodyne system + mixer-preamplifier + amplifier	27
2.4.1. General organization	27

2.4.2. Heterodynes	31
2.4.3. The mixer-preamplifier	34
2.4.4. The amplifier	35
2.5. The drawer	37
2.6. The diffuser	41
2.7. Power supplies	43
2.8. Trials	48
2.8.1. Preparations	48
2.8.2. Measurements	53
2.8.3. Measurement results	55
Chapter 3. Ondes No. 169 (1937)	63
3.1. Presentation of the instrument	63
3.2. Organization of the instrument	63
3.3. The heterodyne system + mixer + LF audio amplifier+ power amplifier	65
3.3.1. General organization	65
3.3.2. Heterodynes	67
3.3.3. The mixer–amplifier	79
3.3.4. The amplifier	81
3.4. The drawer	88
3.4.1. Description	88
3.4.2. Circuit diagram	89
3.4.3. Functional study.	94
3.4.4. The intensity key	96
3.5. The diffuser	101
3.6. The power supply module.	108
3.7. Model	112
3.7.1. Presentation	112
3.7.2. Realization.	112
3.7.3. Tests and measurements	121
Chapter 4. Model '47	125
4.1. Presentation	125
4.2. Synoptic diagram	125
4.3. Operation analysis	125
4.3.1. Heterodynes	125
4.3.2. The mixer	130
4.3.3. First LF	131
4.3.4. The T9 timbre	136
4.3.5. LF power stage	137
4.3.6. Power module	142
4.4. The intensity key, ribbon capacitor and keyboard	142

Chapter 5. Ondes No. 208 (1953)	145
5.1. Introduction	145
5.2. Functional descriptions	146
5.2.1. The unit	146
5.2.2. The block diagram	150
5.2.3. Mechanical/electrical arrangement	150
5.3. Operation analysis	153
5.3.1. Oscillators	153
5.3.2. The fixed-frequency oscillator	154
5.3.3. The variable-frequency oscillator	157
5.4. The ribbon capacitor	161
5.4.1. General provisions	161
5.4.2. Sizing	164
5.4.3. Comments	179
5.5. Keyboard inductors	180
5.5.1. General provisions	180
5.5.2. Sizing	182
5.5.3. The register change	188
5.6. The mixer	190
5.7. 1st LF	193
5.8. LF power stage	196
5.9. Timbre filters	198
5.10. Diffusers	209
5.11. Power supply	209
Chapter 6. Building an Ondes with Vacuum Tubes	213
6.1. Introduction	213
6.2. The electrical schematic	213
6.3. The chassis	214
6.4. The wiring	217
6.5. Special devices	217
6.5.1. The high register tuning capacitor	217
6.5.2. The diapason capacitor	218
6.5.3. The variable tuning inductor of the low register	219
6.5.4. Capacitors for timbre 7	219
6.5.5. HF inductors	220
6.6. The LF output transformer	225
6.7. Generic components	225
6.8. The drawer	225
6.8.1. Introduction	225
6.8.2. The box	225
6.8.3. Switches	227

6.8.4. The quarter-tone control buttons	228
6.8.5. The T8 timbre control knob	230
6.8.6. The power control knob	231
6.8.7. The needle block	232
6.8.8. The intensity key	232
6.8.9. The wiring	232
6.9. The keyboard/ribbon system	234
6.9.1. Introduction	234
6.9.2. The ribbon capacitor	234
6.9.3. The keyboard	241
6.10. The accessories	248
6.10.1. Command buttons	248
6.10.2. Other accessories	250
6.11. Calibration and tuning	254
6.11.1. Introduction	254
6.11.2. Ribbon capacitor calibration	254
6.11.3. Calibrating the keyboard coils	256
6.11.4. Tuning setting	257
6.11.5. The tuning procedure	259
6.12. Some photographs of ondes 2208	260
Chapter 7. Manufacture of the Leather Bag of the Intensity Key and the Ribbon	263
7.1. The intensity key.	263
7.2. The mercury key.	264
7.2.1. Description	264
7.2.2. Operating constraints	264
7.2.3. Realization.	266
7.3. The powder key, first version.	268
7.3.1. Abandonment of the mercury key	268
7.3.2. Description	268
7.3.3. Operating constraints	269
7.3.4. Realization.	269
7.4. The powder key, second version	270
7.4.1. Description	270
7.4.2. Operating constraints	271
7.4.3. Realization.	271
7.5. The powder key, third version	272
7.5.1. Description	272
7.5.2. Operating constraints	272
7.5.3. Realization.	273
7.6. The powder key, fourth version	275
7.6.1. Description	275

7.6.2. Operating constraints	276
7.6.3. Realization.	276
7.7. Other powder bags.	277
7.7.1. Introduction	277
7.7.2. The pedal	277
7.7.3. The knee lever.	278
7.8. Intensity key and gesture control	280
7.9. Manufacturing a powder bag	282
7.9.1. Introduction	282
7.9.2. Problem	283
7.9.3. Manufacturing the mixture.	283
7.9.4. Manufacturing the powder bag	285
7.10. Ribbon manufacturing	288
7.10.1. Introduction	288
7.10.2. Problem.	291
7.10.3. Ribbon manufacturing	291
Chapter 8. Transistorization	297
8.1. Introduction	297
8.2. The support.	297
8.3. The problems of transistorization	299
8.4. Compatible transistor experimental ondes.	301
8.4.1. Introduction	301
8.4.2. Diagram of the HF sub-assembly	301
8.4.3. The LF subset	302
8.4.4. Power supplies	303
8.5. Tests	304
References.	305
Index.	307